

## Simulation Lab: Resistance in Series and Parallel Circuits

**Purpose:** To determine the relationship between voltage drop and current in both parallel and series circuits.

**Materials:** Online simulation -

[http://phet.colorado.edu/simulations/sims.php?sim=Circuit\\_Construction\\_Kit\\_DC\\_Only](http://phet.colorado.edu/simulations/sims.php?sim=Circuit_Construction_Kit_DC_Only)

### Part A – Resistance in a Series Circuit

\*\*\*\*\* reminder  $R_T = V_T/I_T$

1. Create a circuit with two resistors connected to a battery all in series.

Voltage (V)		Current (A)		Resistance ( $\Omega$ )	
$V_1$	4.5	$I_1$	.45	$R_1$	10
$V_2$	4.5	$I_2$	.45	$R_2$	10
$V_T$	9	$I_T$	.45	$R_T$	20

2. Create a circuit with three resistors connected to a battery all in series.

Voltage (V)		Current (A)		Resistance ( $\Omega$ )	
$V_1$	3	$I_1$	.3	$R_1$	10
$V_2$	3	$I_2$	.3	$R_2$	10
$V_3$	3	$I_3$	.3	$R_3$	10
$V_T$	9	$I_T$	.3	$R_T$	30

### Part B – Resistance in a Parallel Circuit

1. Create a circuit with two resistors connected in parallel to a battery.

Voltage (V)		Current (A)		Resistance ( $\Omega$ )	
$V_1$	9	$I_1$	.9	$R_1$	10
$V_2$	9	$I_2$	.9	$R_2$	10
$V_T$	9	$I_T$	1.8	$R_T$	5

2. Create a circuit with three resistors connected in parallel to a battery.

Voltage (V)		Current (A)		Resistance ( $\Omega$ )	
$V_1$	9	$I_1$	.9	$R_1$	10
$V_2$	9	$I_2$	.9	$R_2$	10
$V_3$	9	$I_3$	.9	$R_3$	10
$V_T$	9	$I_T$	2.7	$R_T$	3.3

**Analysis:**

1. As more resistors are added in series what happens to the total resistance?

total resistance increases

2. As more resistors are added in parallel what happens to the total resistance?

total resistance decreases