

Summary: Series and Parallel Circuits

	Series	Parallel
Diagram		
Description		
Voltage		
Current		
Resistance		
Brightness of light when more bulbs added		
Brightness of light when more energy added		